

Course Code : EE 614


Department: Electrical Engineering

Instructor Name: Jayanta Mukherjee


Email: jayanta@ee.iitb.ac.in

Lecture 4


Problems Realizing LC Matching Network

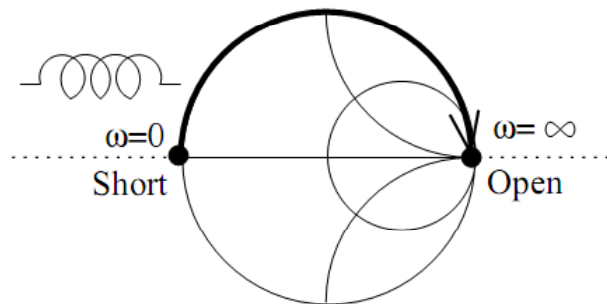


Ideal L

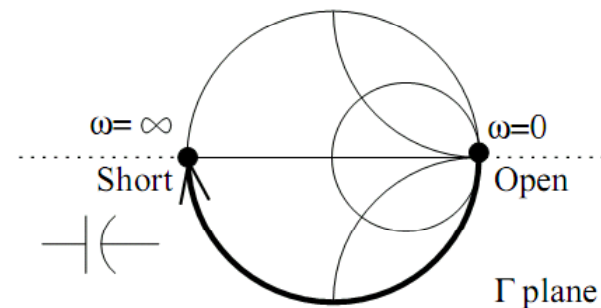

Ideal C

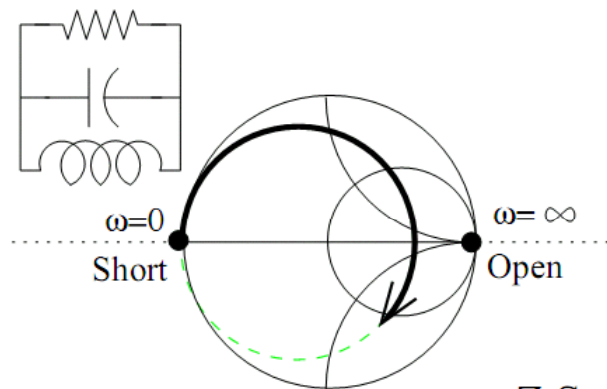


Real L

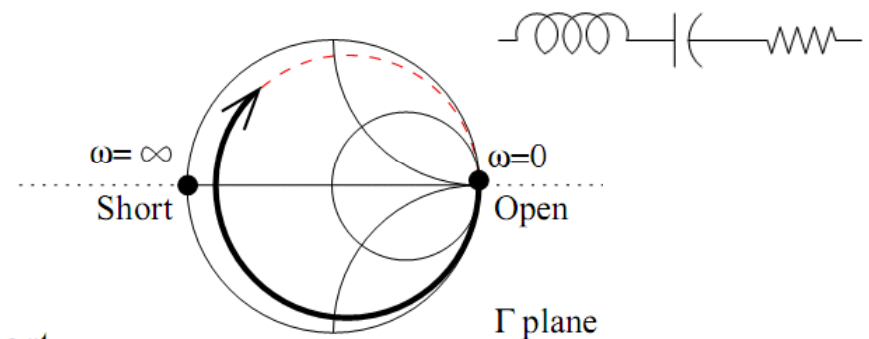

Real C

Microstrip matching network

Microstrip line:

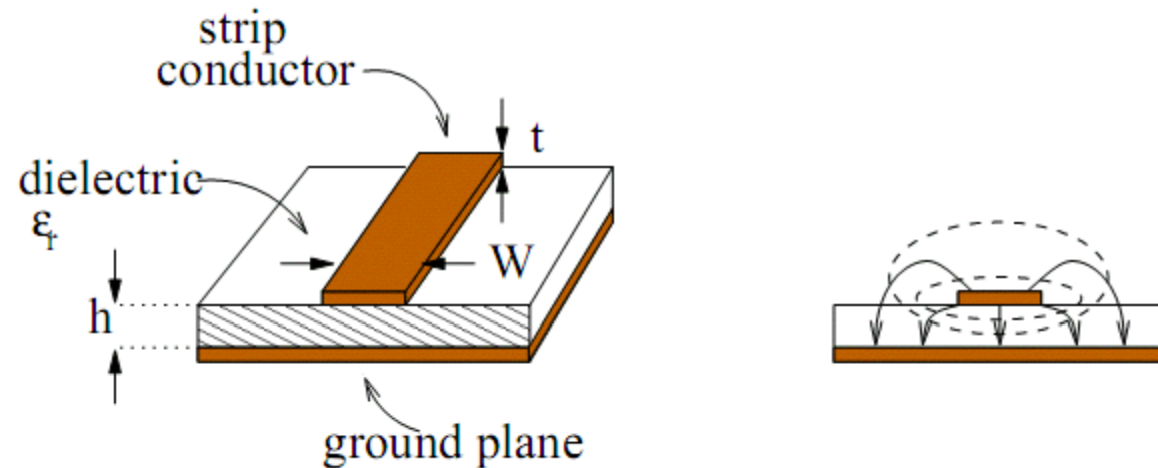

Characteristic impedance of quasi - TEM mode :

$$Z_0 = \frac{1}{V_p C} \quad \text{with} \quad V_p = \frac{c}{\sqrt{\epsilon_{r,eff}}}$$


V_p is the phase velocity, ϵ_{eff} is the effective relative dielectric constant :

$$1 < \epsilon_{r,eff} < \epsilon_r$$

Various Substrates used in Microstrip lines

Material Name	Material type	Price (Rs/feet ²)	Frequency	Dielectric Constant	Dielectric Loss tangent
FR4	Epoxy	150(60mils)	0.9	4.0-4.7 (Not Stable)	0.02
ROGERS Duroid	PTFE teflon	2600	2-10	2.33	0.0012
Alumina	Al ₂ O ₃	HIGH	10	9.5-10	0.0004
Quartz	SiO ₂	HIGH	10	3.8	0.0001
III-V RFIC	GaAs Si	HIGH	10 10	13.2 11.9	0.00056 0.004

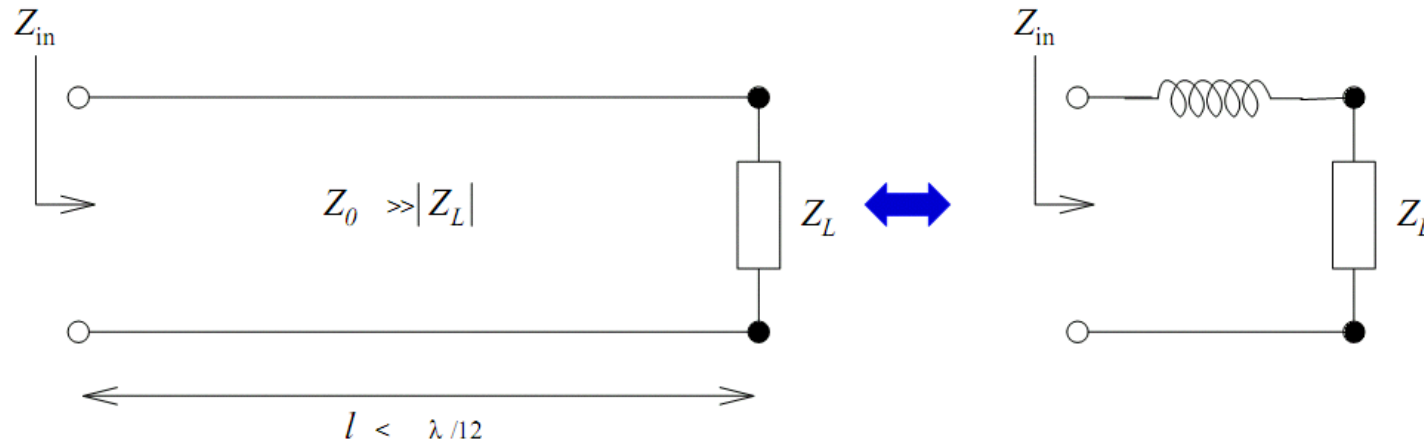
Properties of high impedance line of Short length



$$\begin{aligned}
 Z_{in} &= Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \\
 &\approx Z_0 \frac{Z_L + jZ_0 \beta l}{Z_0 + jZ_L \beta l} \quad \text{for } \beta l < \frac{\pi}{6} \quad \text{or} \quad l < \frac{\lambda}{12} \\
 &\approx Z_L + jZ_0 \beta l = Z_L + j\omega L \quad \text{for } Z_0 > 3 \times |Z_L|
 \end{aligned}$$

where $L = \frac{Z_0 l}{v_p}$ using $\beta = \frac{\omega}{v_p}$

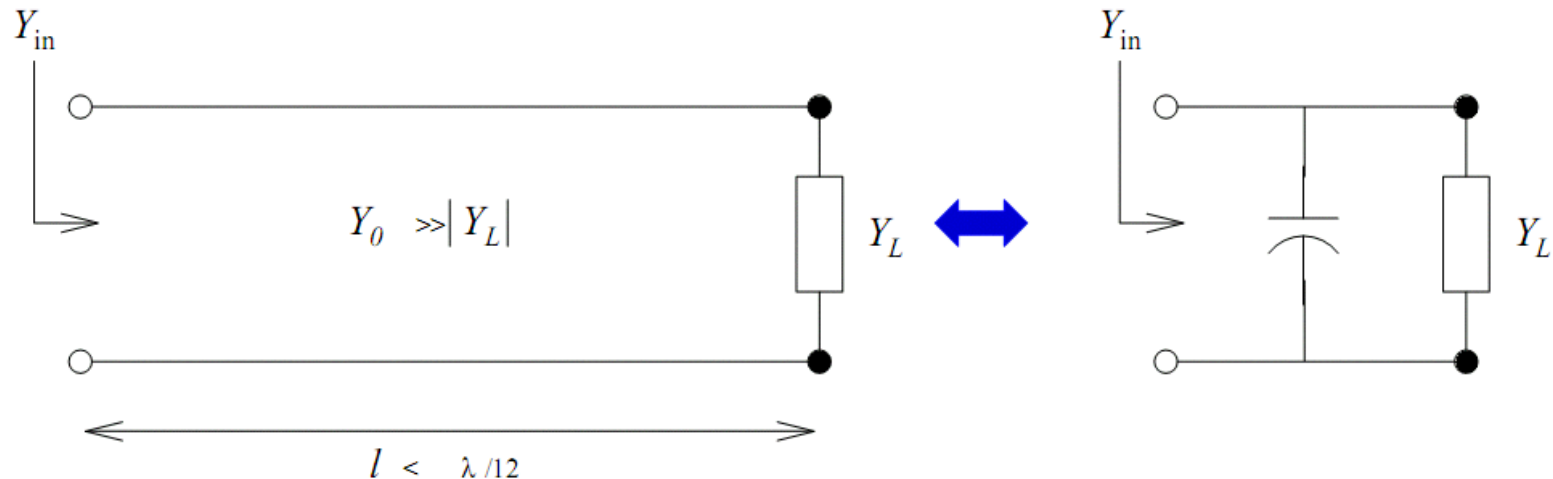Properties of Low impedance line of Short length







$$Y_{in} = Y_0 \frac{Y_L + jY_0 \tan \beta l}{Y_0 + jY_L \tan \beta l}$$

$$\approx Y_0 \frac{Y_L + jY_0 \beta l}{Y_0 + jY_L \beta l} \quad \text{for } \beta l < \frac{\pi}{6} \quad \text{or } 1 < \frac{\lambda}{12}$$


$$\approx Y_L + jY_0 \beta l = Y_L + j\omega C \quad \text{for } Y_0 > 3 \times |Y_L|$$

where $C = \frac{Y_0 l}{v_p}$ using $\beta = \frac{\omega}{v_p}$

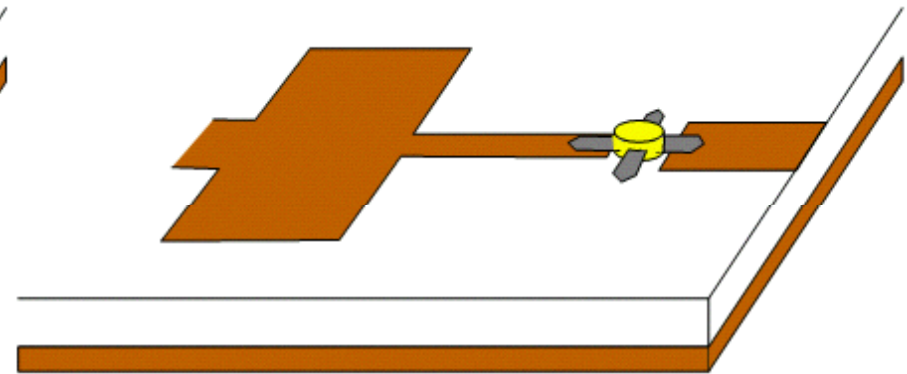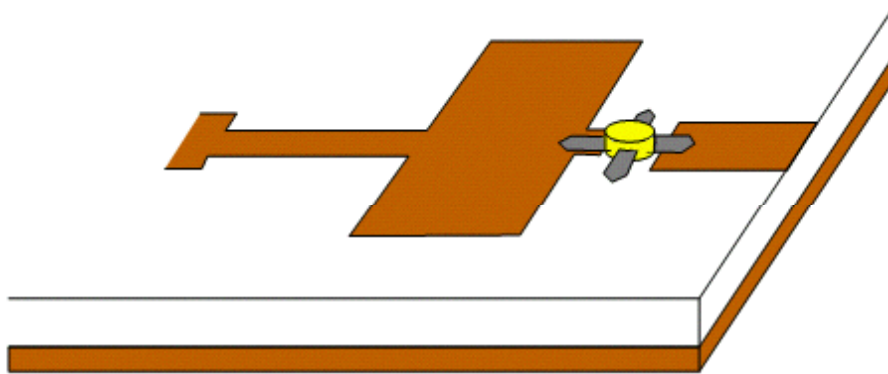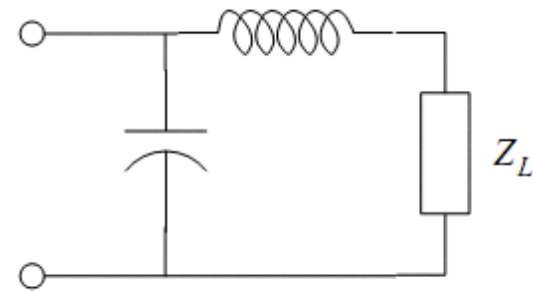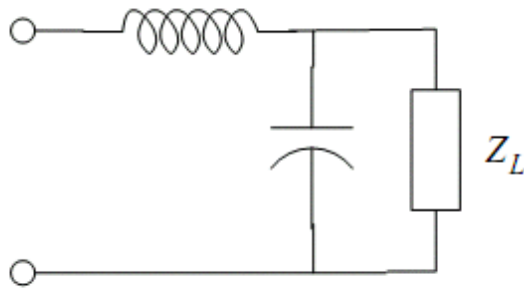Realization of LC Matching Network With Microstrip




Design of a Stub Tuner

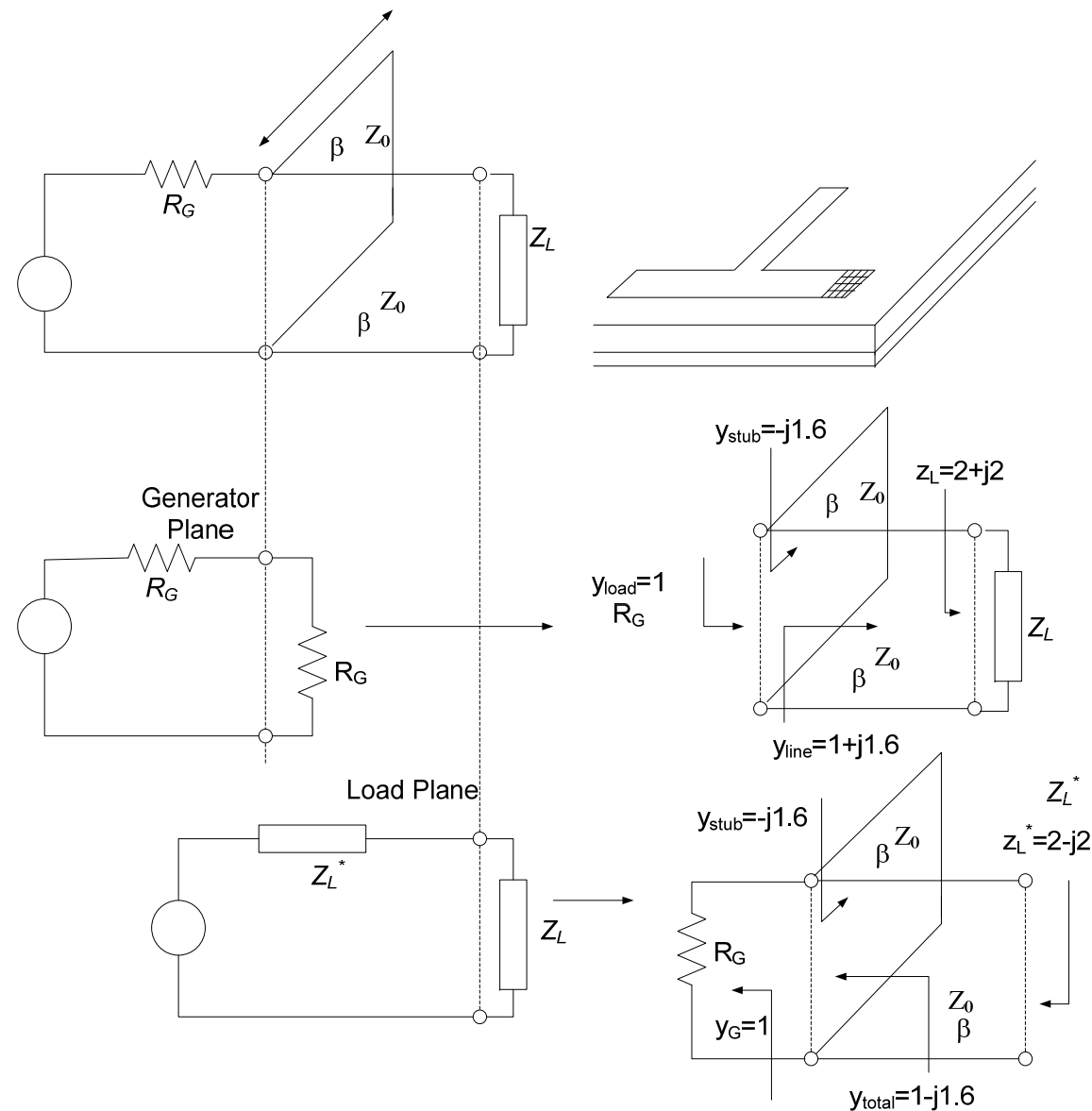

Design Using Generator Plane

Consider the load: $Z_L = 100 + j100$

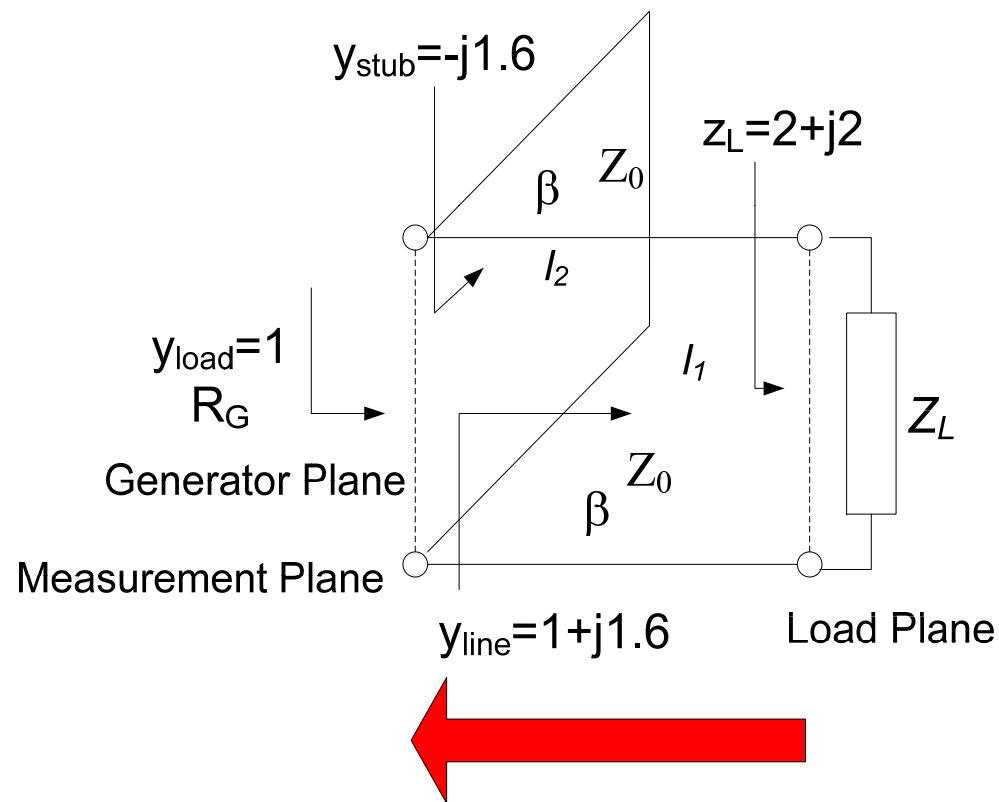Using $Z_0 = 50$ ohms we have $z_L = 2 + j2$




Solution

$$I_1 = 0.2193\lambda, I_2 = 0.089\lambda$$

Moving towards generator


Design Using Generator Plane

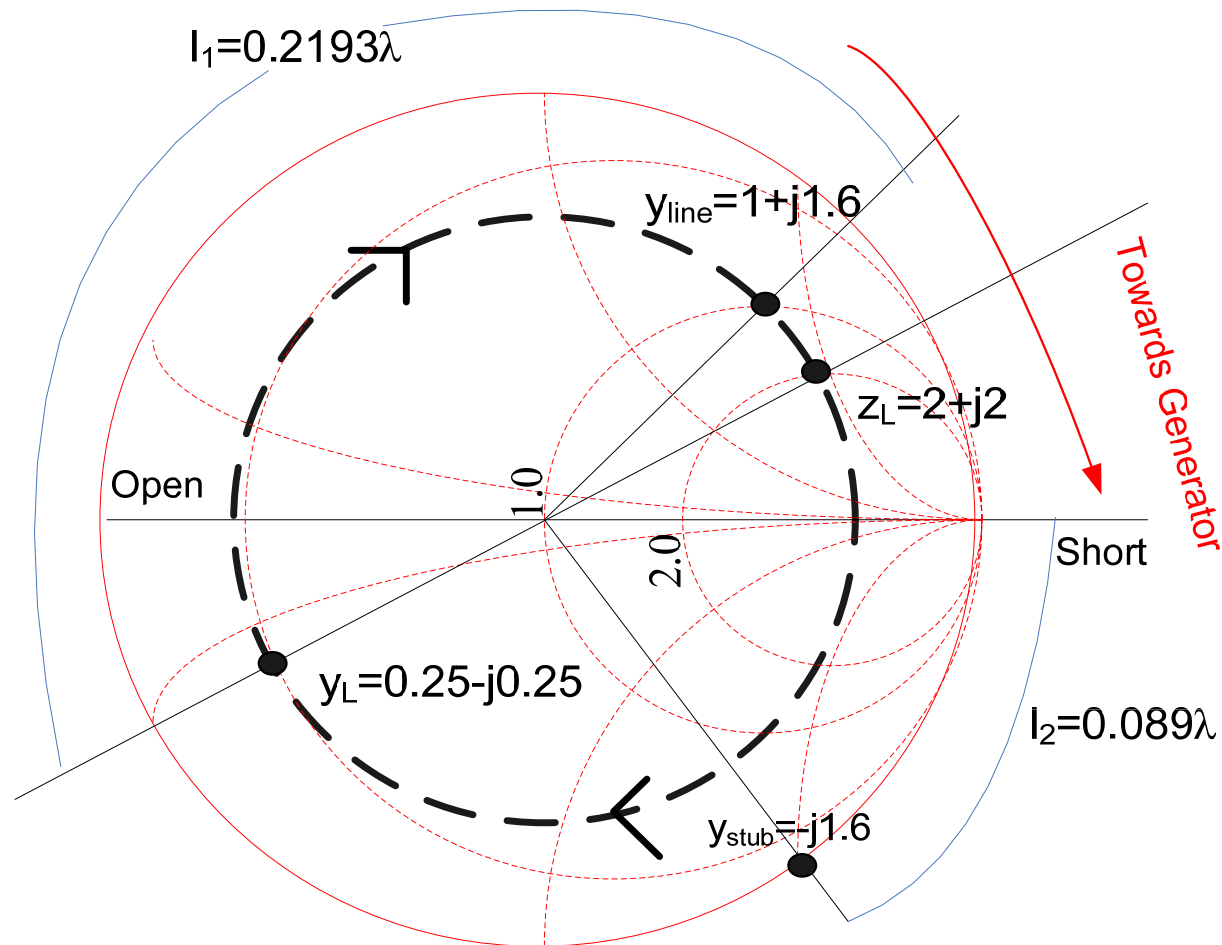

Design Using Load Plane

Consider the load: $Z_L = 100 + j100$

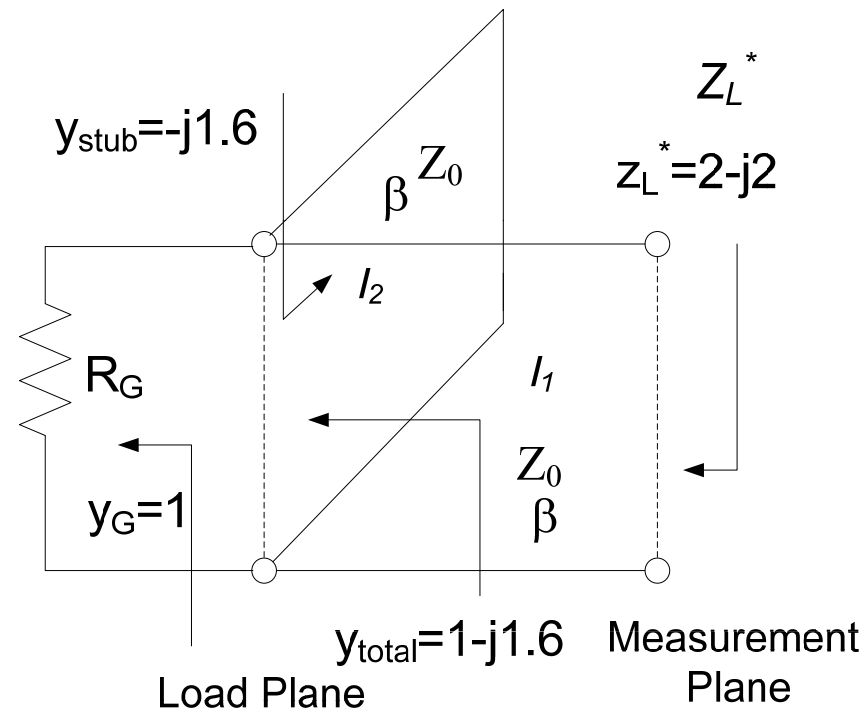
Using $Z_0 = 50$ ohms we have $z_L^* = 2 - j2$



Solution

$$l_1 = 0.2193\lambda, l_2 = 0.089\lambda$$

Design Using Load Plane

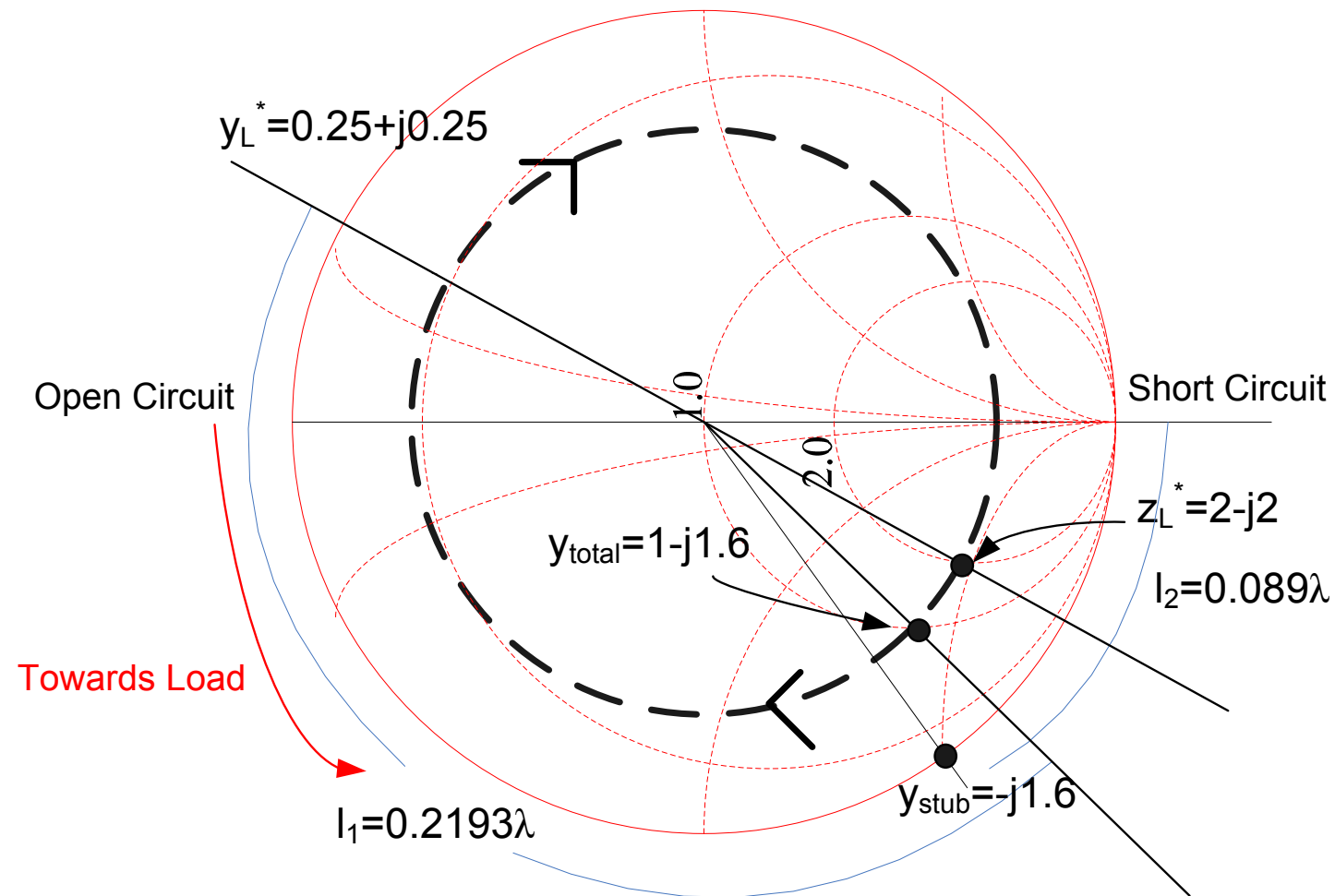

Signal Flow Graphs


- S-parameters were introduced in Chapter 1 to represent 2-port (can be generalized to N-port networks)
- As we design amplifiers we need to analyze bigger circuits realized with multiple building blocks

Flow Graph techniques will provide us:


- an analysis technique applicable to S parameters
- the means to visualize the power flow in a circuit

Signal Flow Graphs

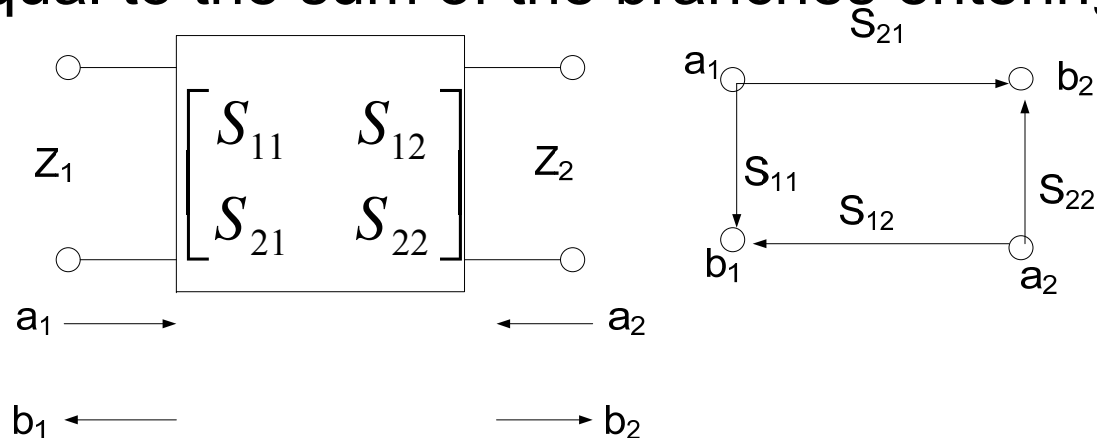- Each variable is designated as a node
- The S parameters and reflection coefficients are represented by branches
- Branches enter dependent variable nodes and emanate from independent variable nodes. The independent/dependent variable nodes are the incident/reflected waves respectively.
- A node is equal to the sum of the branches entering it



Focus on Amplifier Network

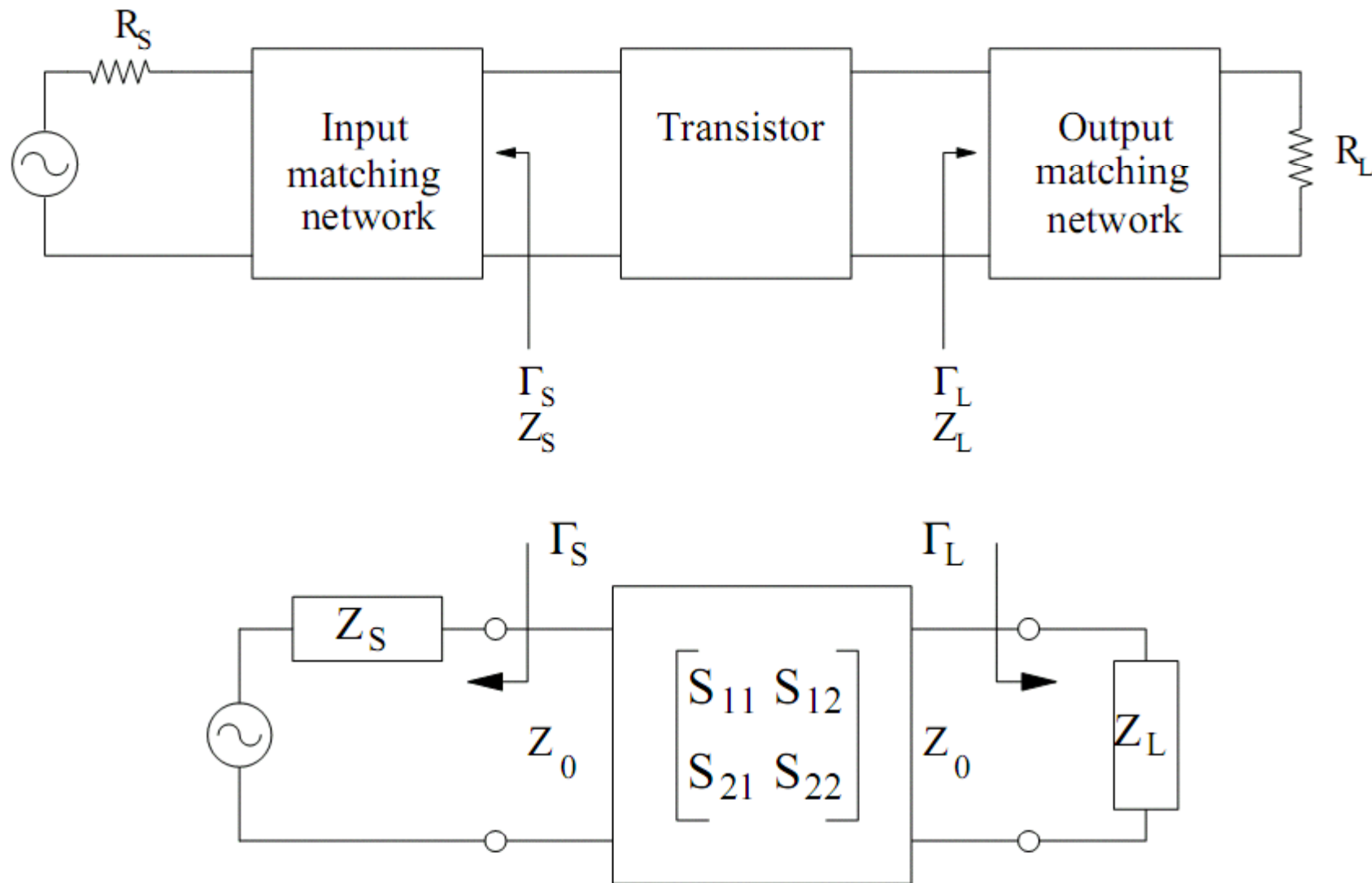

Flow Graph for a Generator

- A basic circuit we need to be analyzed is given below.



Starting from : $V_g = E_s - I_1 Z_s$ and divide by $\sqrt{Z_0}$

$$\frac{V_g}{\sqrt{Z_0}} = \frac{E_s}{\sqrt{Z_0}} - \frac{\sqrt{Z_0} I_1}{Z_0} Z_s$$

$$a_1 + b_1 = \frac{E_s}{\sqrt{Z_0}} - \frac{Z_s}{Z_0} (a_1 - b_1)$$

$$a_1 \left[1 + \frac{Z_s}{Z_0} \right] = \frac{E_s}{\sqrt{Z_0}} + b_1 \left[1 - \frac{Z_s}{Z_0} \right]$$
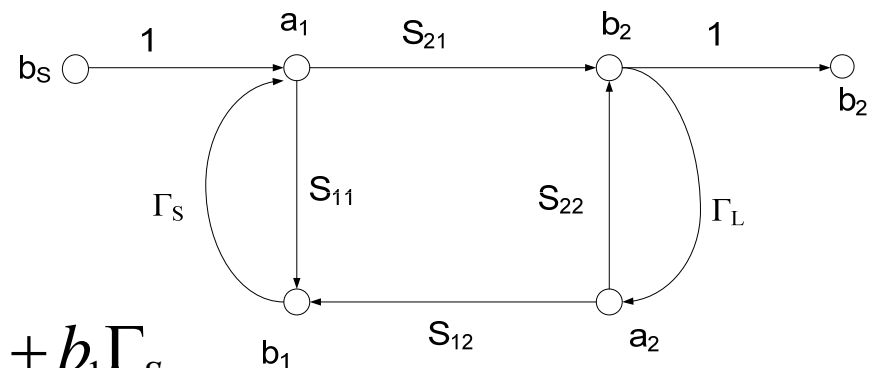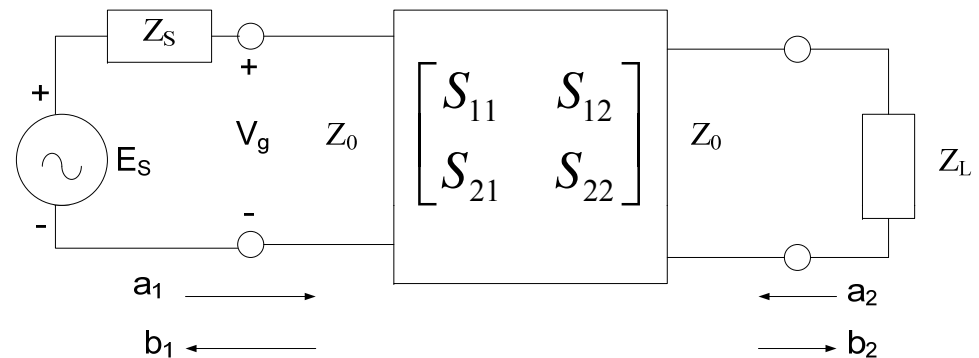
$$a_1 = \underbrace{\frac{\sqrt{Z_0}}{Z_0 + Z_s} E_s}_{b_s} + b_1 \underbrace{\frac{Z_s - Z_0}{Z_s + Z_0}}_{\Gamma_s} = b_s + b_1 \Gamma_s$$



Mason Semantic

Path: continuous succession of branches traversed in their indicated direction, no node being encountered more than once.

Forward Path: Path connecting input to output nodes.

Input Node: A node having only out-going branches.

Output Node: A node having only in-going branches.

Path Gain: Product of the branch multiplier.

Loop: Path which originates and terminates at the same node, no node being encountered more than once.



Loop Gain: Product of the branch multipliers around the loop.

Mason's Rule

- Select input and output nodes
- The gain T from input to output is then: $T = (\sum_k P_k \Delta_k) / \Delta$
with P_k the path gain of the k -th forward path and with Δ and Δ_k given by:
 $\Delta = 1 - (\text{sum of all individual loop gains})$
+ (sum of the loop gain products of all possible combinations of two non-touching loops)
- (sum of the loop gain products of all possible combinations of three non-touching loops)
+ (sum of the loop gain products of all possible combinations of four non-touching loops)
-

Δ_k = value of Δ using loops not touching the k -th path

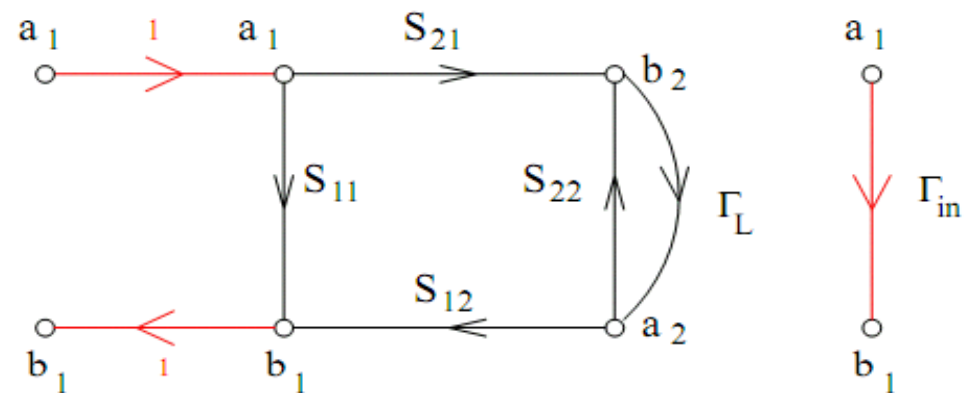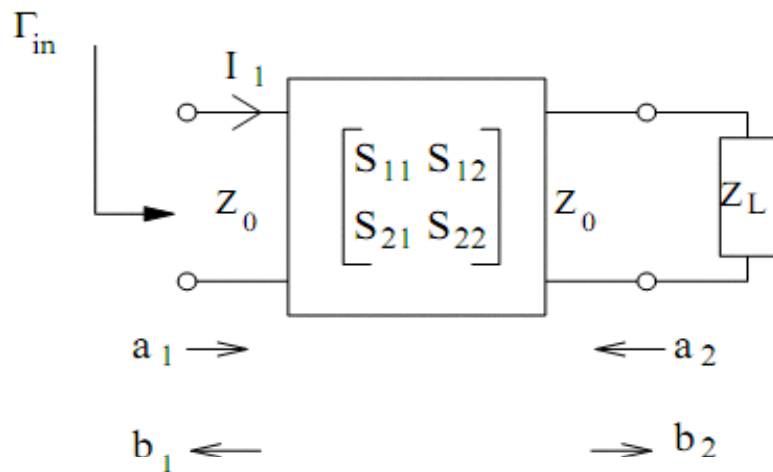Application: Input Reflection Coefficient of a loaded 2-Port Network



- How many paths ?
- How many loops ?

Input Reflection Coefficient of a loaded 2-Port Network

$$\Gamma_{in} = \frac{b_1}{a_1} = \frac{P_1 \Delta_1 + P_2 \Delta_2}{\Delta}$$

Path 1: $P_1 = S_{11}$



Path 2: $P_2 = S_{21} \Gamma_L S_{12}$

Determinant: $\Delta = 1 - S_{22} \Gamma_L$


Determinant 1: $\Delta_1 = 1 - S_{22} \Gamma_L$

Determinant 2: $\Delta_2 = 1$
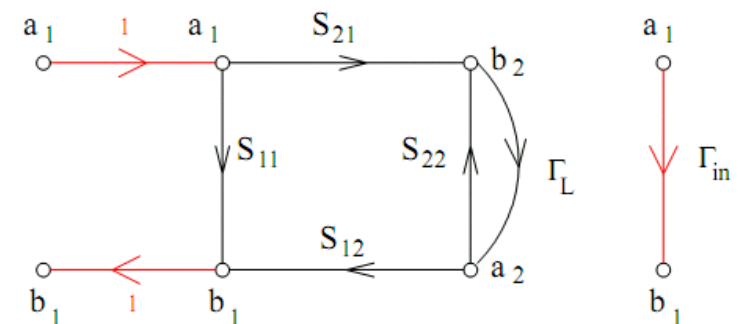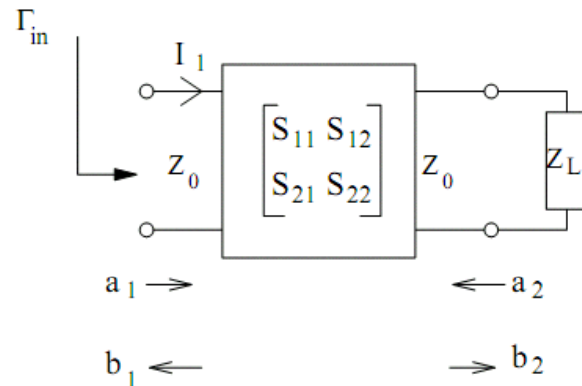
$$\Gamma_{in} = S_{11} + \frac{S_{12} \Gamma_L S_{21}}{1 - S_{22} \Gamma_L}$$



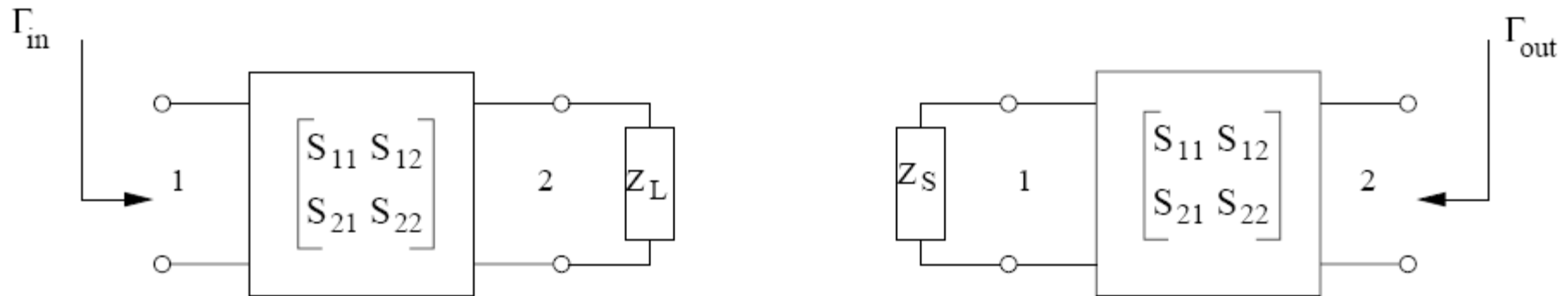Transmission Coefficient of a loaded 2-Port Network



$$T_{21} = \frac{b_2}{a_1} = \frac{P_1 \Delta_1}{\Delta}$$


Path 1: $P_1 = S_{21}$

Determinant: $\Delta = 1 - S_{22}\Gamma_L$

Determinant 1: $\Delta_1 = 1$

$$T_{21} = \frac{b_2}{a_1} = \frac{S_{21}}{1 - S_{22}\Gamma_L}$$

Power Gain

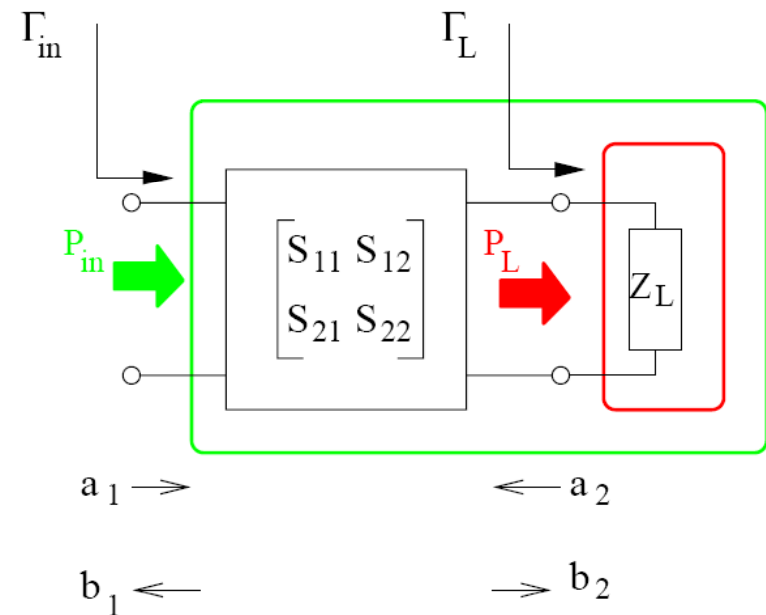


Power Gain :

$$G_p = \frac{\text{Power Delivered to the Load}}{\text{Power Delivered to the Network}} = \frac{P_L}{P_{in}} = \frac{|b_2|^2 - |a_2|^2}{|a_1|^2 - |b_1|^2}$$

$$= \frac{|b_2|^2}{|a_1|^2} \frac{1 - \left| \frac{a_2}{b_2} \right|^2}{1 - \left| \frac{b_1}{a_1} \right|^2} = \frac{|b_2|^2}{|a_1|^2} \frac{1 - |\Gamma_L|^2}{1 - |\Gamma_{in}|^2} = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

Attributes of Power Gain

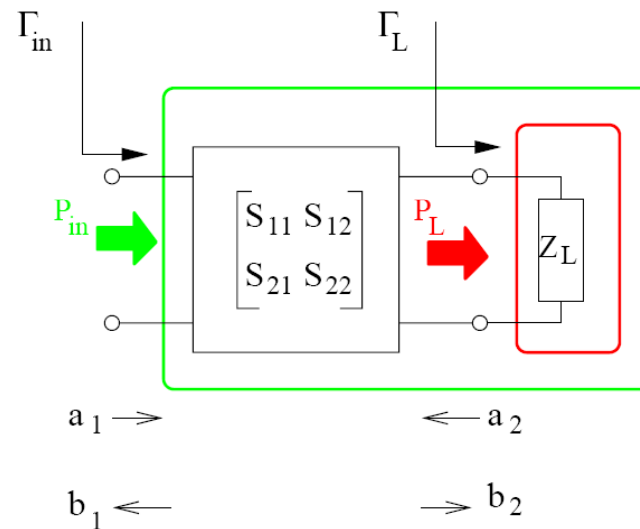

For matched loads we have $\Gamma_L = 0$ and $\Gamma_{in} = S_{11}$ and the power gain is :

$$G_p = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{1 - S_{22}\Gamma_L} = \frac{|S_{21}|^2}{1 - |S_{11}|^2}$$


For lossless device $G_p = 1$ and we have the power conservation relation :

$$1 = |S_{21}|^2 + |S_{11}|^2$$

Features of Power Gain G_p :

- $G_p([S], \Gamma_L)$ finds applications in power amplifier design
- Problem : what if all the power is reflected at the input ?

Transducer Power Gain

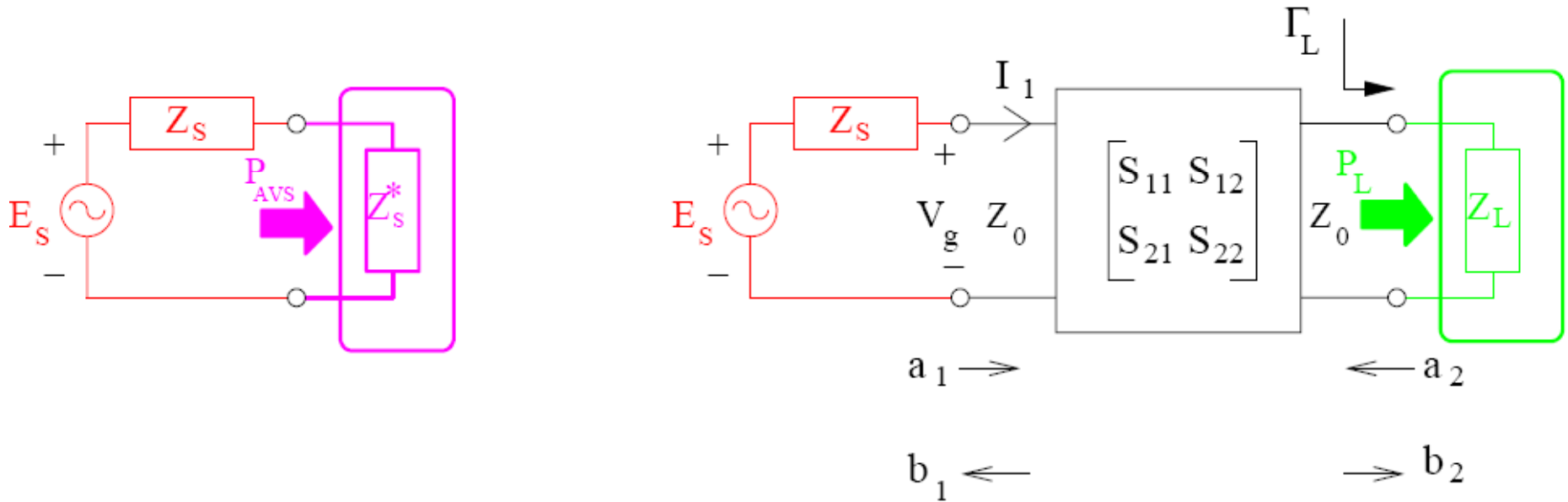

Transducer Power Gain :



$$G_T = \frac{\text{Power delivered to the load}}{\text{Power Available from the source}} = \frac{P_L}{P_{AVS}}$$

Power delivered to the load (rms)

$$P_L = |b_2|^2 - |a_2|^2 = |b_2|^2 (1 - |\Gamma_L|^2)$$

How do we get the Power Available from the source?

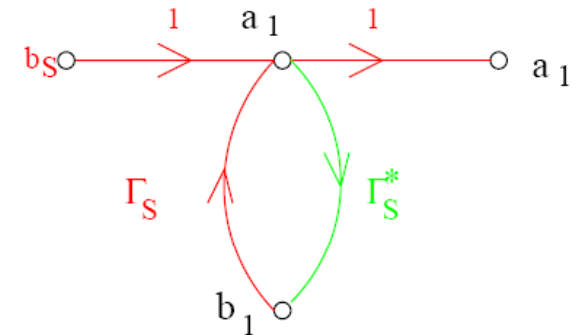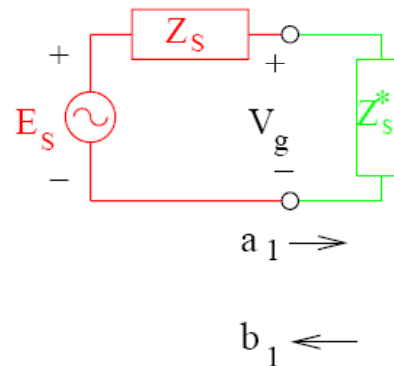Available Power from the source and the resulting G_T



Flow graph solution : $a_1 = \frac{b_s}{1 - |\Gamma_s|^2}$



$$P_{AVS} = |a_1|^2 - |b_1|^2 = |a_1|^2 \left(1 - \frac{|b_1|^2}{|a_1|^2} \right) = |a_1|^2 (1 - |\Gamma_s|^2)$$

$$= \left| \frac{b_s}{1 - |\Gamma_s|^2} \right|^2 (1 - |\Gamma_s|^2) = \frac{|b_s|^2}{1 - |\Gamma_s|^2} \quad \text{since } |\Gamma_s| < 1$$

Transducer Power Gain :

$$G_T = \frac{P_L}{P_{AVS}} = \left| \frac{b_2}{b_s} \right|^2 (1 - |\Gamma_L|^2) (1 - |\Gamma_s|^2) \quad \text{where we need } \frac{b_2}{b_s}$$


Flow Graph for G_T calculation

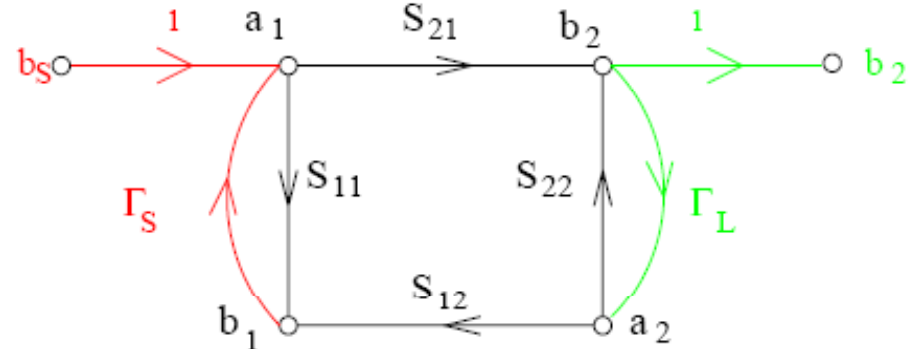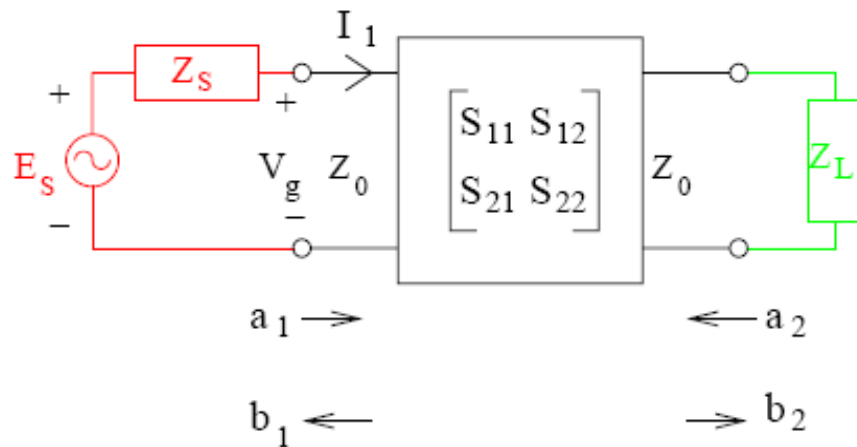

We need to calculate $\frac{b_2}{b_s}$

- How many paths ?
- How many loops ?


Flow Graph for G_T calculation

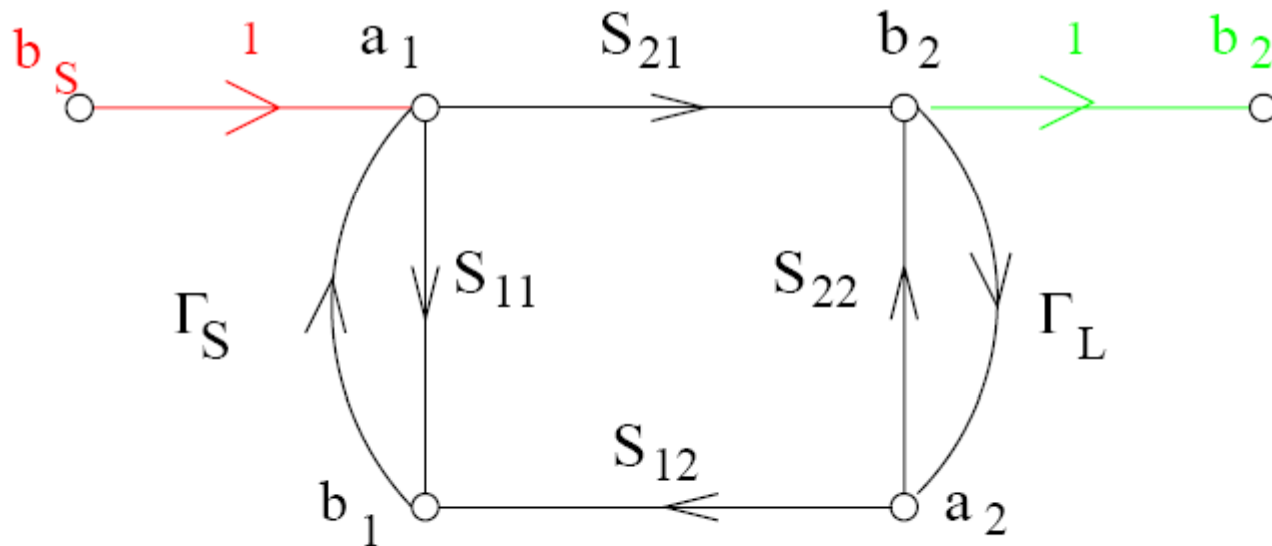

$$\frac{b_2}{b_s} = \frac{P_1 \Delta_1}{\Delta} = \frac{S_{21}}{1 - (\Gamma_S S_{11} + S_{22} \Gamma_L + \Gamma_S S_{21} \Gamma_L S_{12}) + \Gamma_S S_{11} S_{22} \Gamma_L}$$

$$G_T = \left| \frac{b_2}{b_s} \right|^2 (1 - |\Gamma_L|^2) (1 - |\Gamma_S|^2) = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

Attributes of Transducer Power Gain

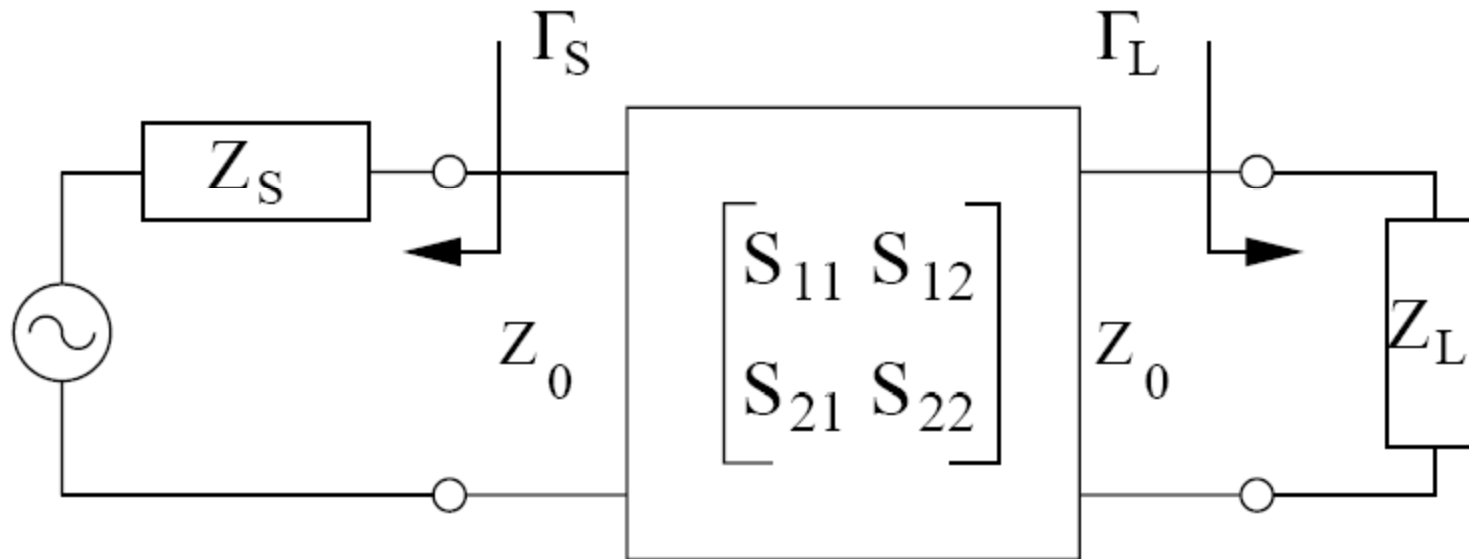


$$G_T = \left| \frac{b_2}{b_s} \right|^2 (1 - |\Gamma_L|^2) (1 - |\Gamma_S|^2) = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2}$$

Properties :

- $G_T([S], \Gamma_S, \Gamma_L)$ function of both source and load impedances
- $G_T = |S_{21}|^2$ for $\Gamma_S = \Gamma_L = 0$ (matched loads at input and output)

Attributes of Transducer Power Gain

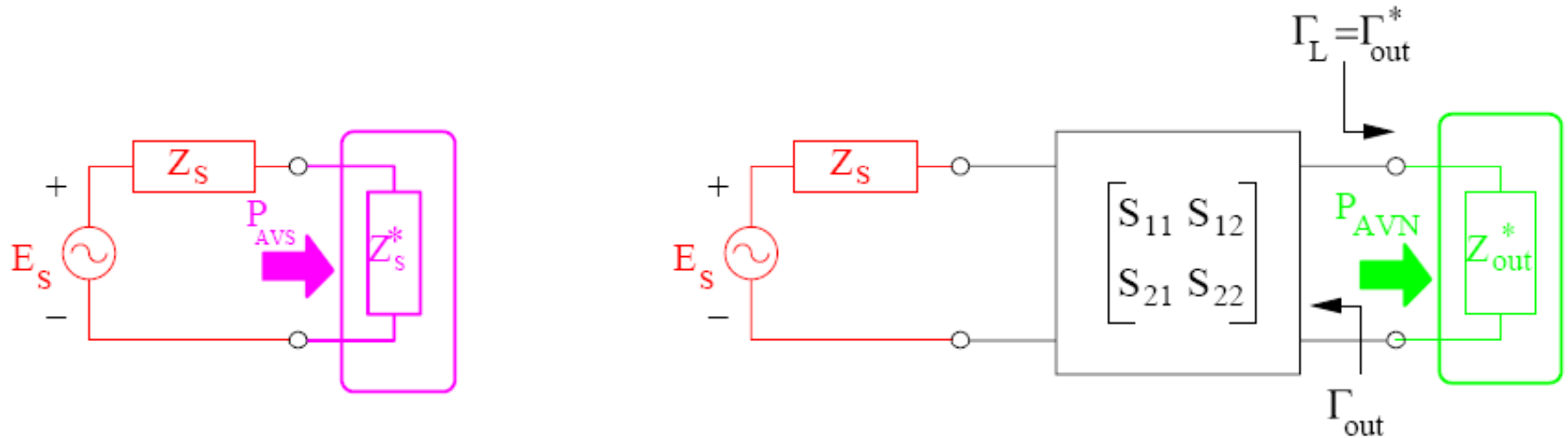


$$G_T = \left| \frac{b_2}{b_s} \right|^2 (1 - |\Gamma_L|^2) (1 - |\Gamma_S|^2) = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11} \Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2}$$

Properties :

- $G_T([S], \Gamma_S, \Gamma_L)$ function of both source and load impedances
- $G_T = |S_{21}|^2$ for $\Gamma_S = \Gamma_L = 0$ (matched loads at input and output)

Available Power Gain

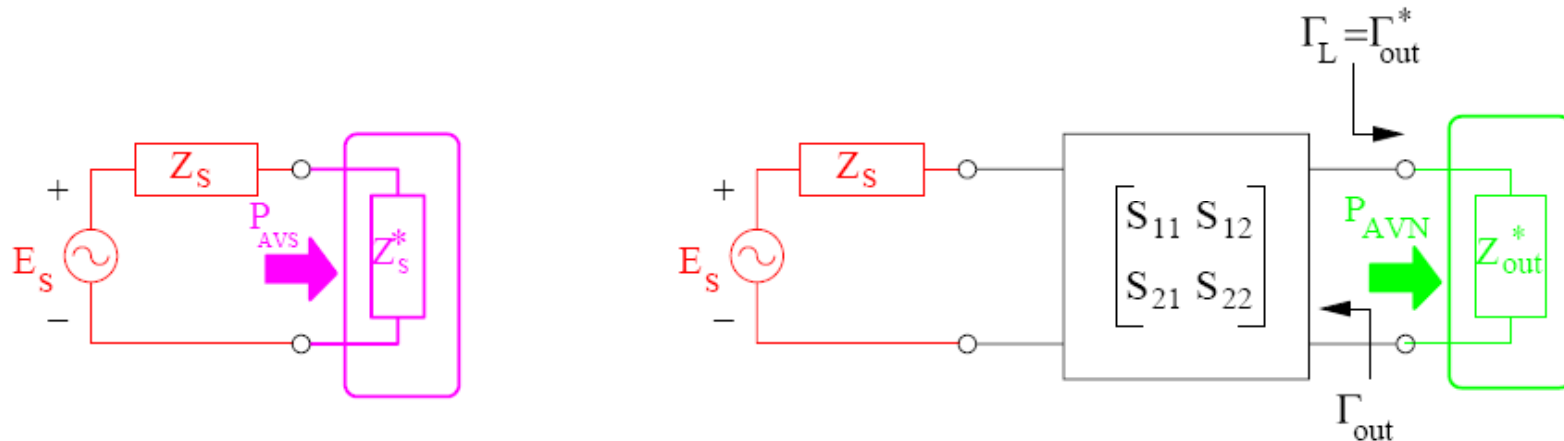

$$\begin{aligned}
 G_A &= \frac{\text{Power Available from the Network}}{\text{Power Available from the Source}} = \frac{P_{AVN}}{P_{AVS}} \\
 &= G_T \big|_{\Gamma_L = \Gamma_{out}^*} \\
 &= \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{|1 - \Gamma_{out}|^2}
 \end{aligned}$$

Properties :

- $G_A([S], \Gamma_S)$ finds applications in LNA design
- Assumes a conjugate match at the output