

$$\Rightarrow a_1 = \frac{\sqrt{Z_0}}{Z_0 + Z_S} E_S + b_1 \left(\frac{Z_S - Z_0}{Z_S + Z_0} \right)$$

$$b_S = \frac{\sqrt{Z_0} E_S}{Z_0 + Z_S} \quad (\text{comes purely from generator})$$


$$\Rightarrow a_1 = b_S + b_1 T_S$$

$$T_{out} = \frac{b_1}{a_2} = \frac{S_{22} + S_{12} T_S S_{21}}{1 - S_{11} T_S} \quad (\text{find}) \rightarrow T_{out} \text{ is the dual of } T_{in}$$

$$\left\{ \begin{array}{l} a_2 = T_L b_2 \\ b_2 = T_{out} a_2 \end{array} \right\}$$

FLOW GRAPHS

a 's & b 's are taken as nodes of graph.

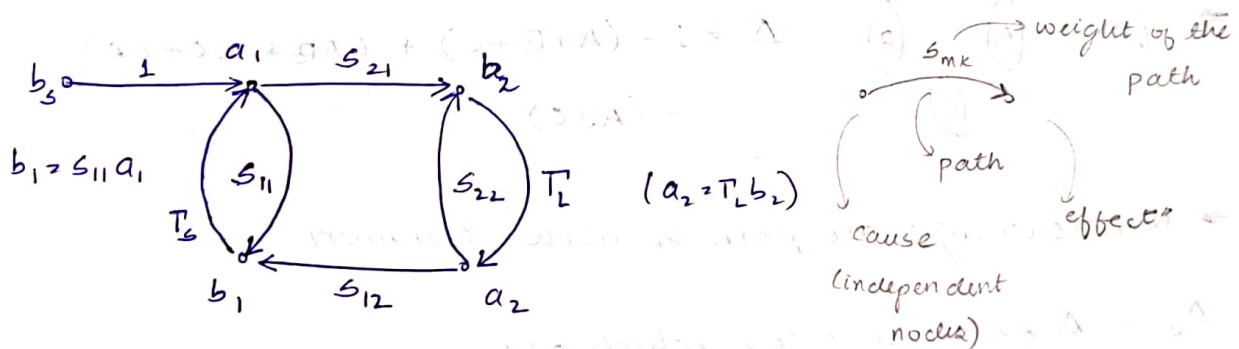

a_1, a_2 : independent variables

[Ex: if port 2 by a_2 we have an effect b_2]

\rightarrow loop (can't cross the same node twice)

Path should be in one direction

Path from $a_1 \rightarrow b_1$

(i) S_{11}

(ii) $S_{21} \rightarrow T_L \rightarrow S_{12}$

Mason's rule

$$\text{Gain (ratio)} = \frac{\sum P_k \Delta_k}{\Delta}$$

- where, P_k = ^{total gain}
number of forward path b/w the quantities
whose ratio is to be found

eg: $P_1 (a_1 \rightarrow b_1) = S_{11}$

$P_2 (a_1 \rightarrow b_1) = S_{21} T_L S_{12}$

- $\Delta = 1 - (\text{sum of individual loop gains})$
(same for all gain ratios) + (sum of ^{non-touching} loop gain products taken 2 at a time)
- (sum of ^{non-touching} loop gain products taken 3 at a time)

eg: $\Delta = 1 - (S_{11} T_3 + S_{22} T_L + S_{21} S_{12} T_L T_3) + (S_{11} T_3 S_{22} T_L)$

\Rightarrow for $\begin{pmatrix} A \\ B \\ C \end{pmatrix}$ $\Delta = 1 - (A+B+C) + (AB+BC+CA) - (ABC)$

\rightarrow Non-touching: no path or nodes common

- $\Delta_k = \Delta$ for those loops which are not touching that forward path

$\Rightarrow \Delta_1 = 1 - S_{22} T_L$

$\Delta_2 = 1$

$\Rightarrow \frac{b_1}{a_1} = \frac{S_{11} (1 - S_{22} T_L) + S_{21} T_L S_{12}}{1 - (S_{11} T_3 + S_{22} T_L + S_{12} S_{21} T_L T_3) + (S_{11} S_{22} T_3 T_L)}$

if $T_3 = 0$


$$\frac{b_1}{a_1} = \frac{S_{11} (1 - S_{22} T_L) + S_{21} T_L S_{12}}{1 - (S_{22} T_L)}$$

$$\frac{b_1}{a_1} = S_{11} + \frac{S_{21} T_L S_{12}}{1 - S_{22} T_L} \quad (\text{same as before})$$

→ find T_{out}



• ABCD / TRANSMISSION PARAMETERS

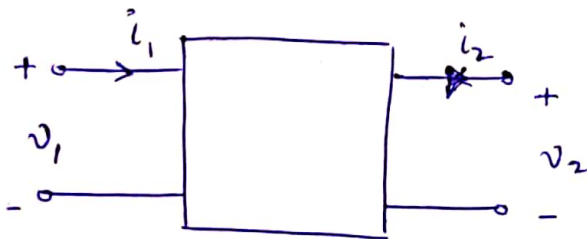

(helpful in cascade network)

$$\begin{bmatrix} V_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ i_2 \end{bmatrix}$$

